

# Introduction to Digital Logic

## EECS/CSE 31L

### Assignment 2: 1-Bit ALU

Prepared by: Jack Melcher

Student ID: 67574625

EECS Department  
Henry Samueli School of Engineering  
University of California, Irvine

January 28, 2015

## 1 Block Description

Take in two 1-bit values (a and b) and 4 select values in order to perform a variety of operations

## 2 Input/Output Port Description

Port name	Port size	Port Type	Description
A	1	IN	Value of first input
B	1	IN	Value of second input
Cin	1	INOUT	The carry in value
opsel	2 downto 0	IN	Determine which operation to perform in units
mode	1	OUT	Determine whether the output is from arithmetic operation or logic operation
output	1	OUT	The output value of operation
cout	1	OUT	The carry out value

## 3 Design Schematics

### Truth Tables:

ALU Operations

Mode	OPSEL	Micro-operation	Description
0	000	$a+b$	Add
0	001	$a+b'$	Sub with borrowed carry
0	010	$a$	Move
0	011	$a+b'+1$	Sub
0	100	$a+1$	increment
0	101	$a-1$	decrement
0	110	$a+b+1$	Add & Increment

1	000	a AND b	Bit-wise AND
1	001	a OR b	Bit-wise OR
1	010	a XOR b	Bit-wise Exclusive OR
1	011	a'	Compliment
1	101	shl a	1 Bit Shift Left

Cin table

Opsel	cin	Description
000	0	Add
001	1	Sub with borrowed carry
010	0	Move
011	1	Sub
100	1	increment
101	0	decrement
110	1	Add & Increment

Full Adder

In_0	In_1	Cin	Cout	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Two's Complement Full Adder/Subtractor

In_0	In_1	Cin	Cout	Sum
0	0	0	0	0
0	1	0	0	1
1	0	0	0	1
1	1	0	1	0
0	0	1	1	0
0	1	1	0	1
1	0	1	1	1
1	1	1	1	0

### Boolean Expressions:

Full Adder

$$\text{Sum} = (A \oplus B) \oplus \text{Cin}$$


$$\text{Cout} = (A)(B) + (\text{Cin})(A \oplus B)$$

Two's Complement Full Adder

$$\text{Sum} = (A \oplus (B \oplus \text{Cin})) \oplus \text{Cin}$$


$$\text{Cout} = (A)(B \oplus \text{Cin}) + ((\text{Cin})(A \oplus (B \oplus \text{Cin})))$$

**Design:**

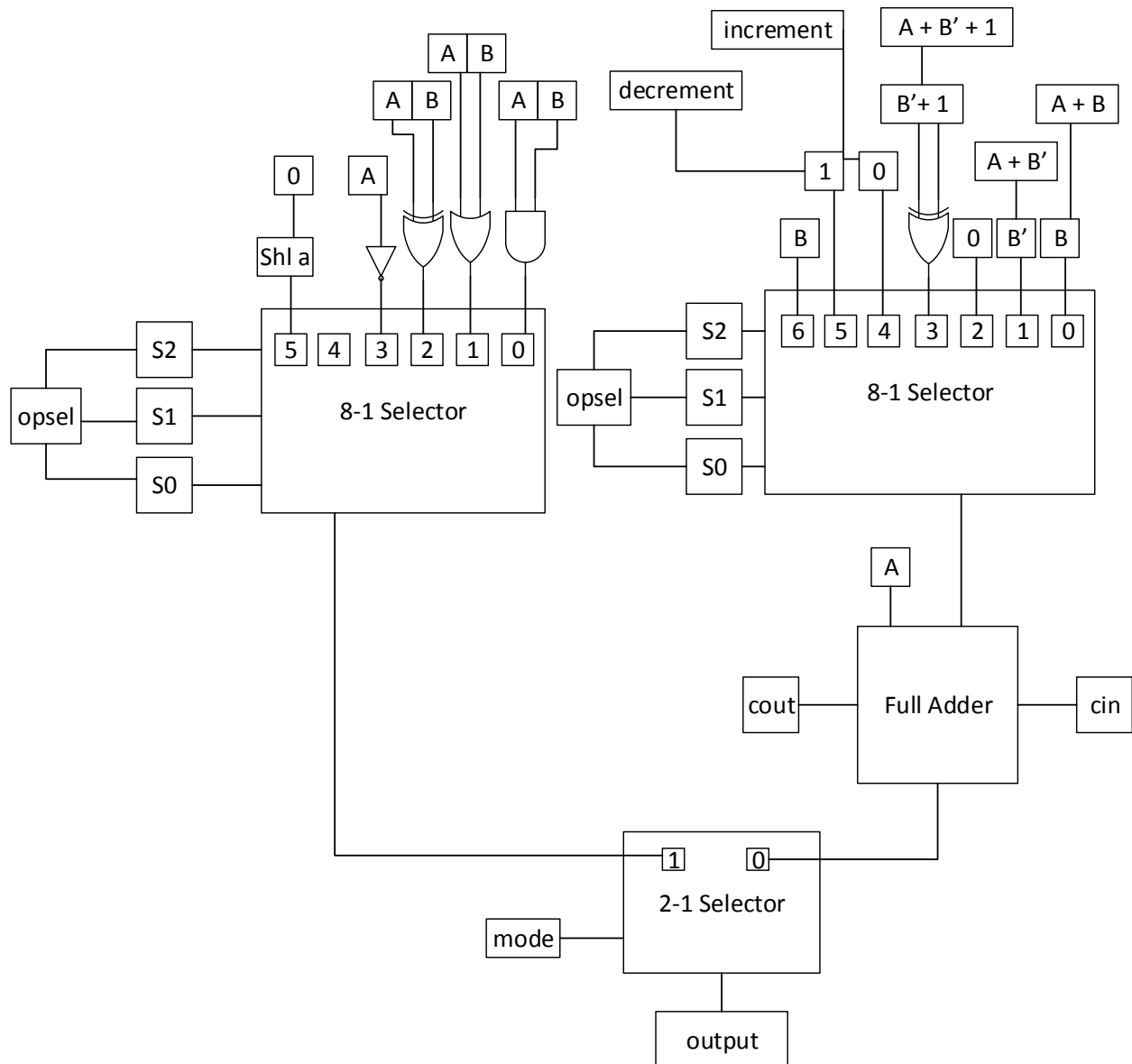


## 4 Compilation

### Arithmetic unit

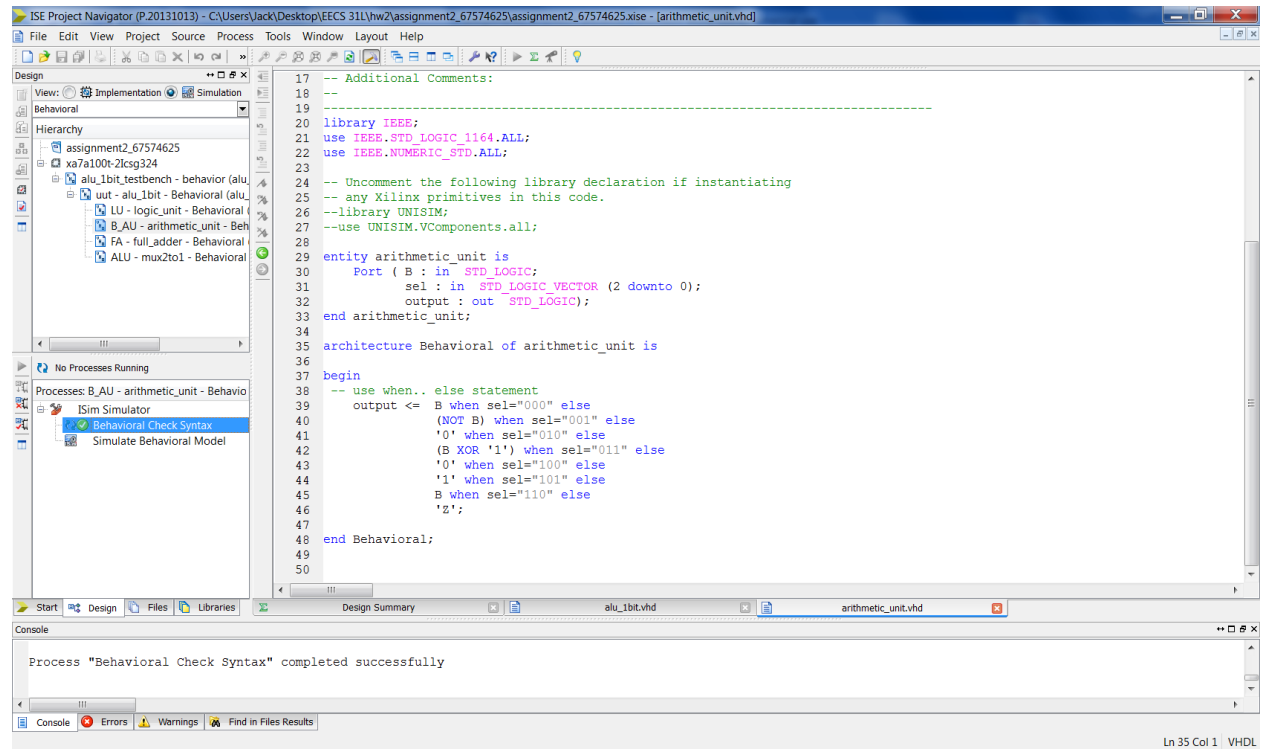

### Full Adder

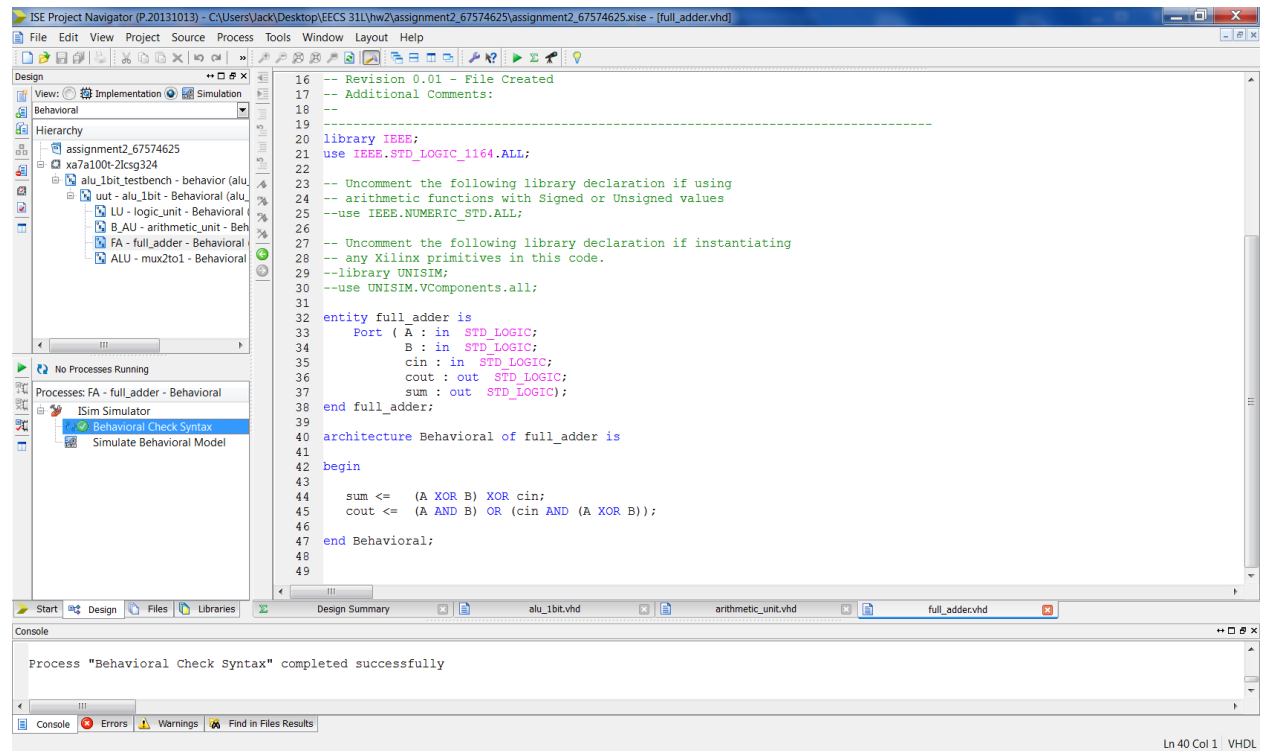

## Logic Unit

The screenshot shows the ISE Project Navigator interface with the 'Logic Unit' VHDL file open. The design hierarchy on the left shows the project structure, including the 'Logic Unit' component. The main editor displays the VHDL code for the 'logic\_unit' entity, which implements a 2-to-1 multiplexer. The code includes library declarations for IEEE and UNISIM, and a behavioral architecture using a 'when..else' statement to select between two inputs based on a selector signal.

```
20 library IEEE;
21 use IEEE.STD_LOGIC_1164.ALL;
22
23 -- Uncomment the following library declaration if using
24 -- arithmetic functions with Signed or Unsigned values
25 --use IEEE.NUMERIC_STD.ALL;
26
27 -- Uncomment the following library declaration if instantiating
28 -- any Xilinx primitives in this code.
29 --library UNISIM;
30 --use UNISIM.VComponents.all;
31
32 entity logic_unit is
33     Port ( A : in  STD_LOGIC;
34           B : in  STD_LOGIC;
35           sel: in  STD_LOGIC;
36           output : out STD_LOGIC);
37 end logic_unit;
38
39
40 architecture Behavioral of logic_unit is
41
42 begin
43     -- use when.. else statement
44     output <= (A AND B) when sel="000" else
45                (A OR B) when sel="001" else
46                (A XOR B) when sel="010" else
47                (NOT A) when sel="011" else
48                shl when sel="101" else
49                'Z';
50
51 end Behavioral;
52
53
```

The console window at the bottom shows the message: "Process 'Behavioral Check Syntax' completed successfully".

Ln 40 Col 1 | VHDL

## Mux 2to1

The screenshot shows the ISE Project Navigator interface with the 'Mux 2to1' VHDL file open. The design hierarchy on the left shows the project structure, including the 'Mux 2to1' component. The main editor displays the VHDL code for the 'mux2to1' entity, which implements a 2-to-1 multiplexer. The code includes library declarations for IEEE and UNISIM, and a behavioral architecture using a 'when..else' statement to select between two inputs based on a selector signal.


```
16 -- Revision 0.01 - File Created
17 -- Additional Comments:
18
19 -----
20 library IEEE;
21 use IEEE.STD_LOGIC_1164.ALL;
22
23 -- Uncomment the following library declaration if using
24 -- arithmetic functions with Signed or Unsigned values
25 --use IEEE.NUMERIC_STD.ALL;
26
27 -- Uncomment the following library declaration if instantiating
28 -- any Xilinx primitives in this code.
29 --library UNISIM;
30 --use UNISIM.VComponents.all;
31
32 entity mux2to1 is
33     Port ( in0 : in  STD_LOGIC;
34           in1 : in  STD_LOGIC;
35           sel : in  STD_LOGIC;
36           output : out STD_LOGIC);
37 end mux2to1;
38
39
40 architecture Behavioral of mux2to1 is
41
42 begin
43     -- use when.. else statement
44     output <= in0 when sel='0' else
45                in1 when sel='1' else
46                'Z';
47
48 end Behavioral;
49

```


The console window at the bottom shows the message: "Process 'Behavioral Check Syntax' completed successfully".

Ln 39 Col 1 | VHDL

# ALU

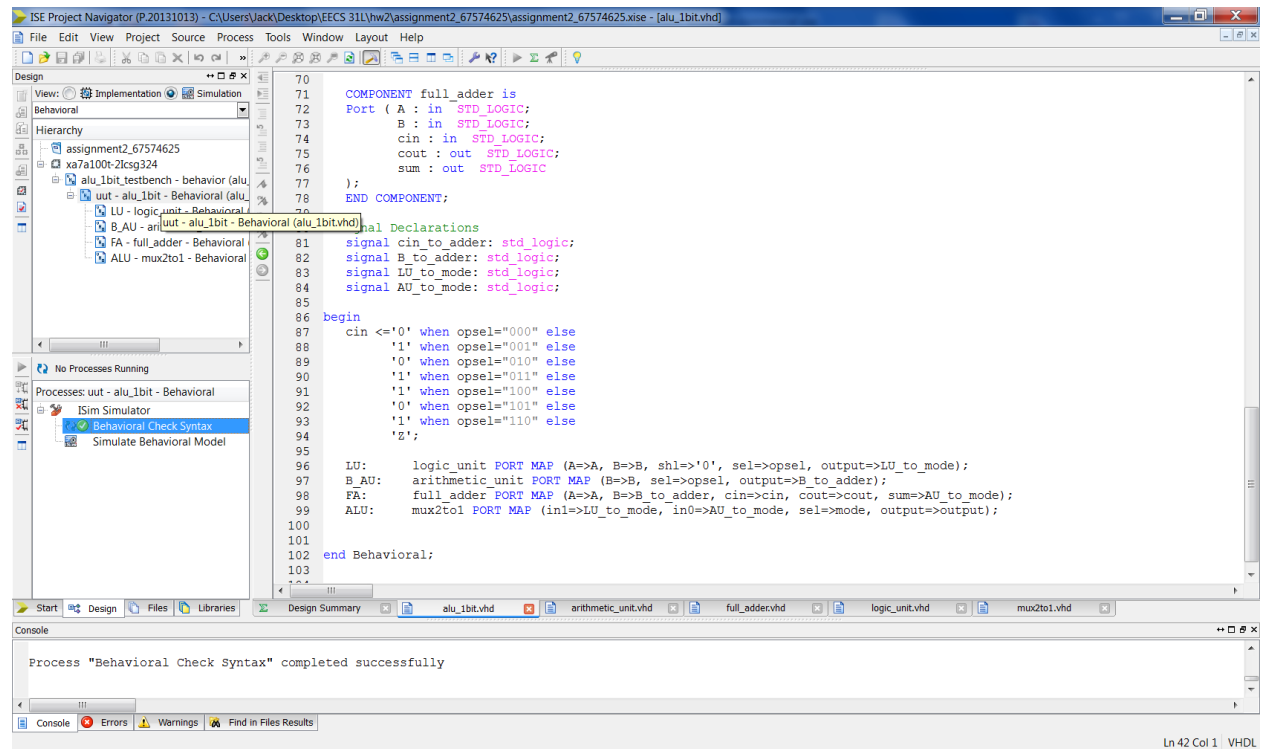

## Testbench

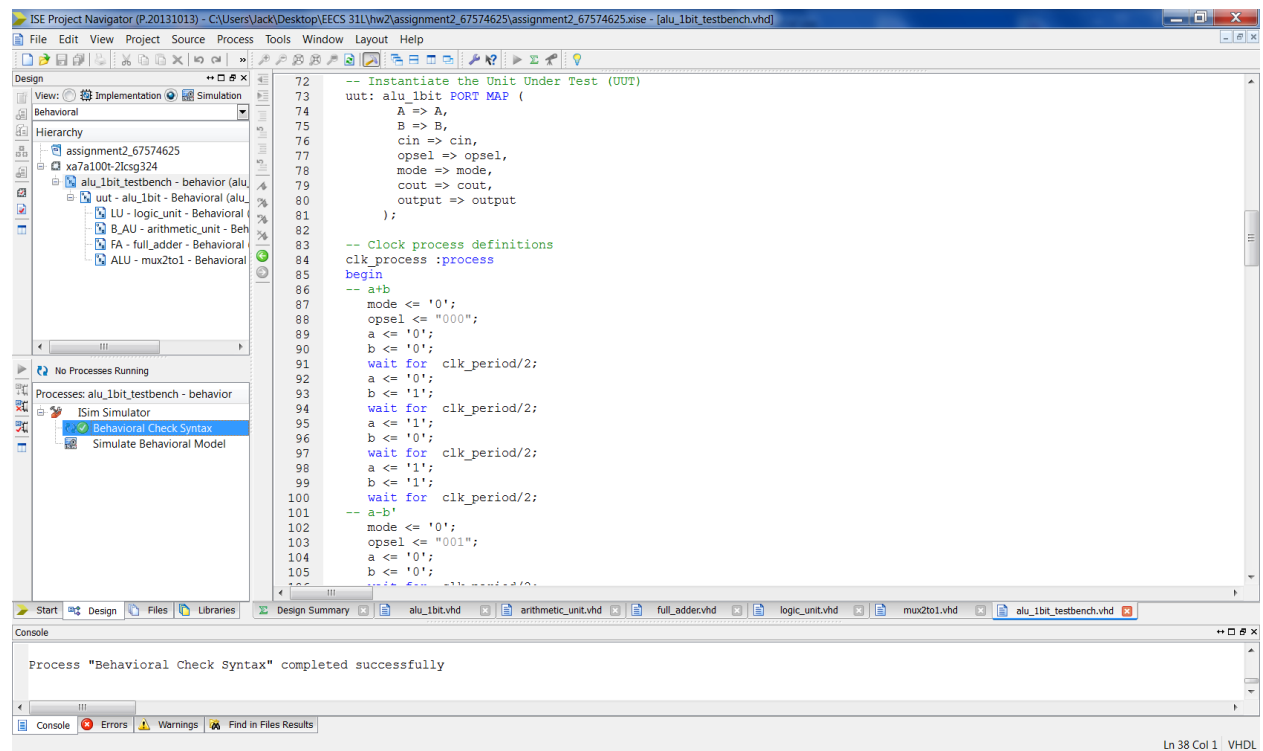

## 5 Elaboration

### Assumptions:

Value of cin

- I change cin from an IN port type to an INOUT port type. This way I could assign it a specific value that correlated to the function.
- This was done in the ALU architecture

Arithmetic

- $a+b$  is just the full adder
- $a+b'$  is just the full adder and will only subtract properly with  $cin = 1$
- $a+b'+1$  subtraction is like two's complement full adder/subtractor;  $cin = 1$  and  $b \text{ XOR } 1$
- Move A will only work properly if  $cin = 0$
- To properly increment a number a 1-bit,  $A = A$ ,  $B = 0$  and  $cin = 1$
- To properly decrement a number a 1-bit,  $A = A$ ,  $B = 1$ , and  $cin = 0$
- To properly add and increment,  $A = A$ ,  $B = B$ , and  $cin = 1$
- For  $a+b+1$  to work properly,  $cin = 1$

Logic

- Because A is only 1-bit, when A is shifted left, a 0 is always shifted in its place.

Regarding how I wrote my vhdl code

- I wrote 4 components and then the top level ALU 1bit
- Arithmetic unit that selects value of b
- Full adder to handle the addition/subtraction
- Logic unit that selects logic operation
- And a 2to1 mux that uses mode to pick the final output.

### Errors and Challenges:

- I had to learn how to use multiple vhdl modules, signals, component declarations, and port mapping in order for my alu to function properly
- Ran into errors about with setting up proper signaling and connecting components properly
- I was confused on how to properly set cin value within ALU and not the testbench. I went through a lot of trial and error in order to figure this out. I ended up changing cin

## Simulation Log:

Started : "Simulate Behavioral Model".

Determining files marked for global include in the design...

Running fuse...

Command Line: fuse -intstyle ise -incremental -lib secureip -o {C:/Users/Jack/Desktop/EECS 31L/hw2/assignment2\_67574625/alu\_1bit\_testbench\_isim\_beh.exe} -prj {C:/Users/Jack/Desktop/EECS 31L/hw2/assignment2\_67574625/alu\_1bit\_testbench\_beh.prj} work.alu\_1bit\_testbench { }

Running: C:\Xilinx\14.7\ISE\_DS\ISE\bin\nt64\unwrapped\fuse.exe -intstyle ise -incremental -lib secureip -o C:/Users/Jack/Desktop/EECS 31L/hw2/assignment2\_67574625/alu\_1bit\_testbench\_isim\_beh.exe -prj C:/Users/Jack/Desktop/EECS 31L/hw2/assignment2\_67574625/alu\_1bit\_testbench\_beh.prj work.alu\_1bit\_testbench

ISim P.20131013 (signature 0x7708f090)

Number of CPUs detected in this system: 4

Turning on mult-threading, number of parallel sub-compilation jobs: 8

Determining compilation order of HDL files

Parsing VHDL file "C:/Users/Jack/Desktop/EECS 31L/hw2/assignment2\_67574625/mux2to1.vhd" into library work

Parsing VHDL file "C:/Users/Jack/Desktop/EECS 31L/hw2/assignment2\_67574625/logic\_unit.vhd" into library work

Parsing VHDL file "C:/Users/Jack/Desktop/EECS 31L/hw2/assignment2\_67574625/full\_adder.vhd" into library work

Parsing VHDL file "C:/Users/Jack/Desktop/EECS 31L/hw2/assignment2\_67574625/arithmetic\_unit.vhd" into library work

Parsing VHDL file "C:/Users/Jack/Desktop/EECS 31L/hw2/assignment2\_67574625/alu\_1bit.vhd" into library work

Parsing VHDL file "C:/Users/Jack/Desktop/EECS 31L/hw2/assignment2\_67574625/alu\_1bit\_testbench.vhd" into library work

Starting static elaboration

Completed static elaboration

Compiling package standard

Compiling package std\_logic\_1164

Compiling package numeric\_std

Compiling architecture behavioral of entity logic\_unit [logic\_unit\_default]

Compiling architecture behavioral of entity arithmetic\_unit [arithmetic\_unit\_default]

Compiling architecture behavioral of entity full\_adder [full\_adder\_default]

Compiling architecture behavioral of entity mux2to1 [mux2to1\_default]

Compiling architecture behavioral of entity alu\_1bit [alu\_1bit\_default]




Compiling architecture behavior of entity alu\_1bit\_testbench  
 Time Resolution for simulation is 1ps.  
 Waiting for 1 sub-compilation(s) to finish...  
 Compiled 14 VHDL Units  
 Built simulation executable C:/Users/Jack/Desktop/EECS  
 31L/hw2/assignment2\_67574625/alu\_1bit\_testbench\_isim\_beh.exe  
 Fuse Memory Usage: 35992 KB  
 Fuse CPU Usage: 576 ms  
 Launching ISim simulation engine GUI...  
 "C:/Users/Jack/Desktop/EECS  
 31L/hw2/assignment2\_67574625/alu\_1bit\_testbench\_isim\_beh.exe" -intstyle ise -gui -tclbatch  
 isim.cmd -wdb "C:/Users/Jack/Desktop/EECS  
 31L/hw2/assignment2\_67574625/alu\_1bit\_testbench\_isim\_beh.wdb"  
 ISim simulation engine GUI launched successfully


Process "Simulate Behavioral Model" completed successfully

## 6 Waveforms

### Full Waveform Snapshot 1

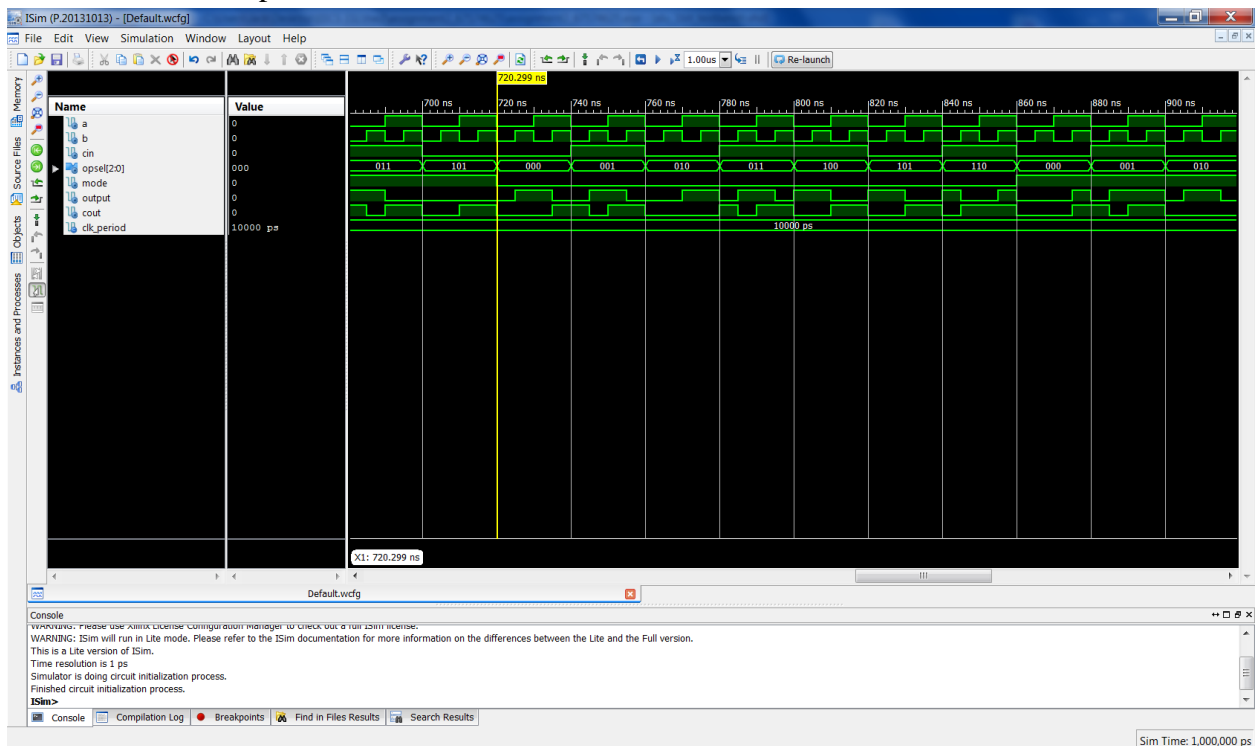


## Full Waveform Snapshot 2

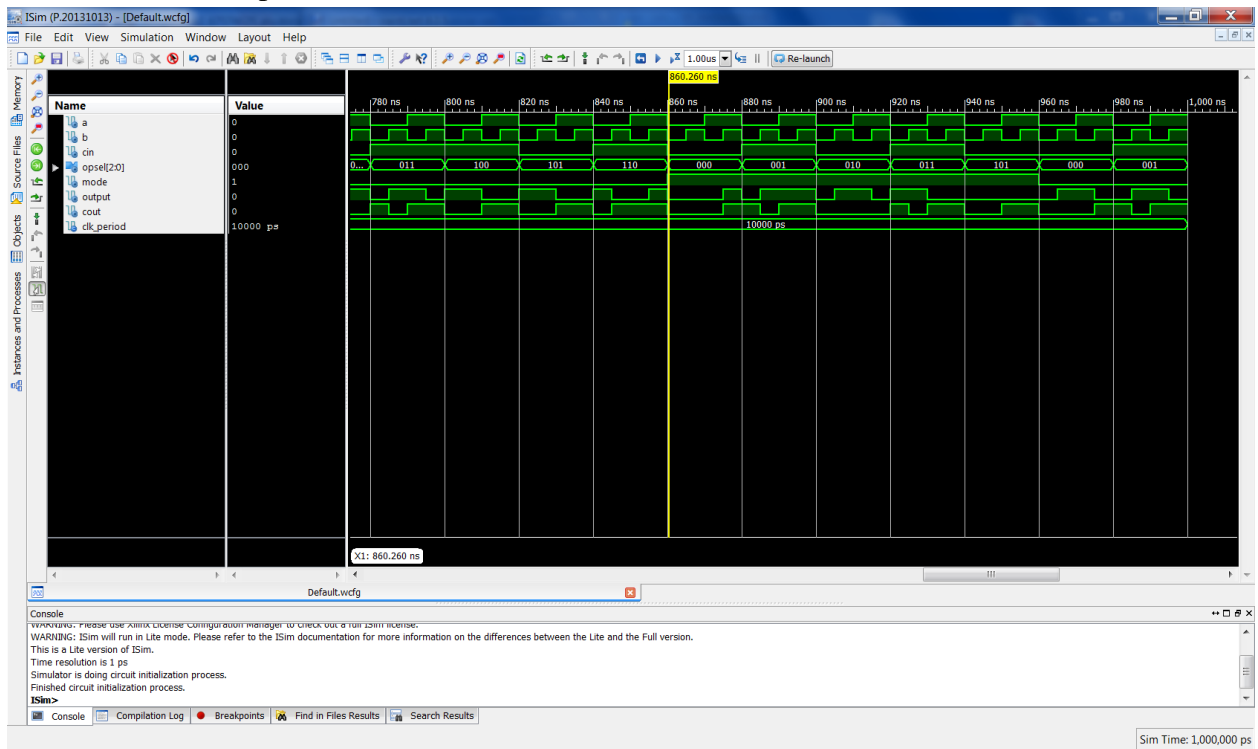


## Snapshots of Waveforms


a+b

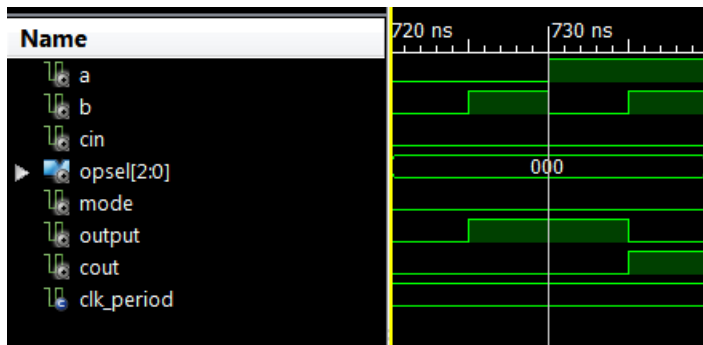


a-b'

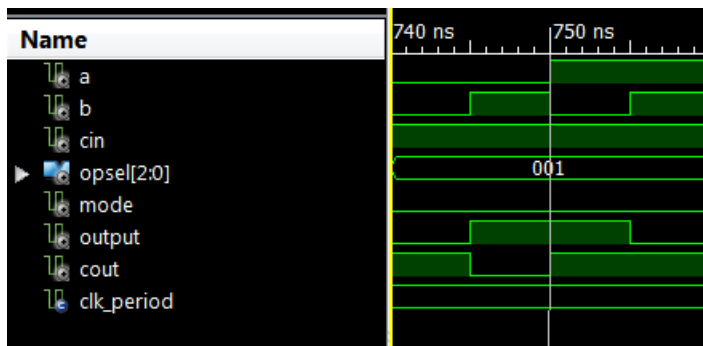


a

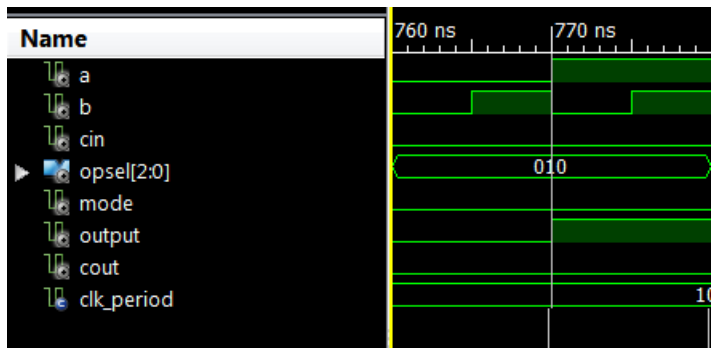


a+b'+1

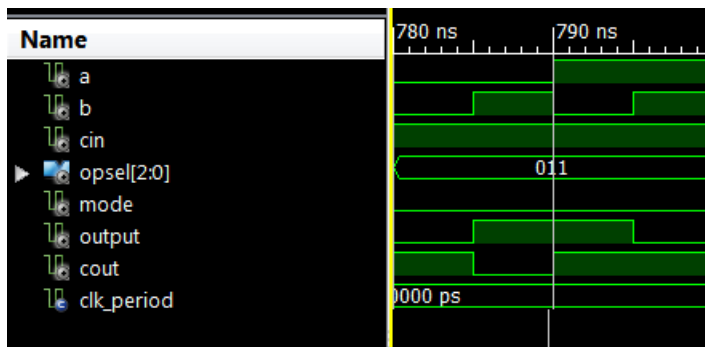


a+1

 


a-1

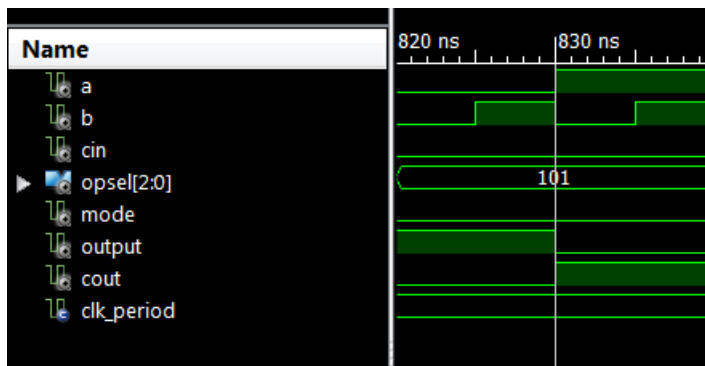


a+b+1

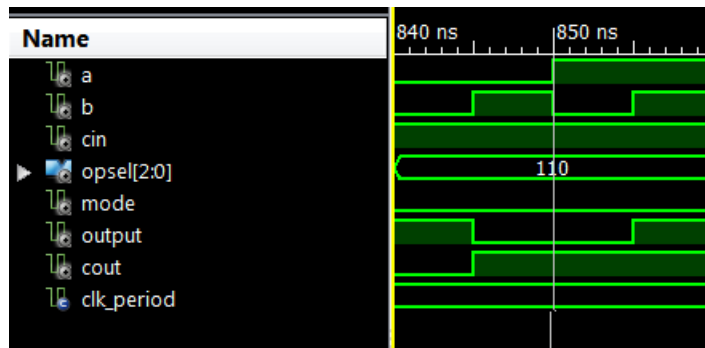


a AND b

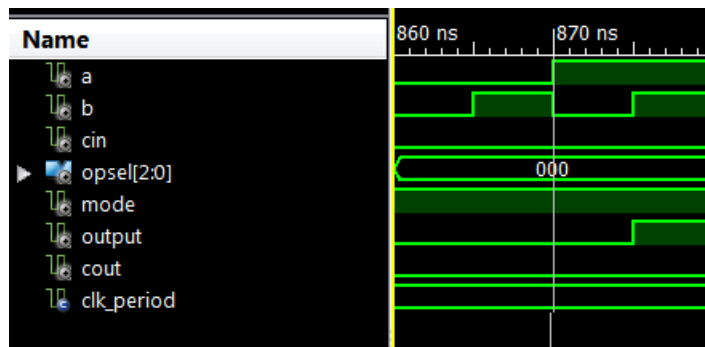


a OR b

 

a XOR b

 

a'

 

shift left a

