

# Introduction to Digital Logic

## EECS/CSE 31L

### Assignment 4: Register

Prepared by: Jack Melcher

Student ID: 67574625

EECS Department  
Henry Samueli School of Engineering  
University of California, Irvine

February 15, 2015

## 1 Block Description

- Construct a register that can be parameterized
- Can load a given input value
- Increment the value stored in the register
- Has an asynchronous reset and synchronous reset

## 2 Input/Output Port Description

Generic Name	Data Type	Default Value	Description
NBIT	INTEGER	32	Size of register

Port name	Port size	Port Type	Description
Clk	1	IN	Triggers the register process
Rst_a	1	IN	Will reset the register when active
Rst_s	1	IN	Will reset the register when active and clock rises
We	1	IN	Enables writing to the register
din	NBIT-1 downto 0	IN	The input value
dout	NBIT-1 downto 0	OUT	The register's stored value


Variable Name	Data Type	Port size	Description
temp	INTEGER	NBIT-1 downto 0	Aids in register process

### 3 Design Schematics

**Truth Table:**


Clk (Rising edge)	Rst_a	Rst_s	inc	we	Function
X	1	X	X	X	Asynchronous Reset
1	0	1	X	X	Synchronous Reset
1	0	0	0	1	Load Input
1	0	0	1	1	Increment Value Stored in Register

**Design:**

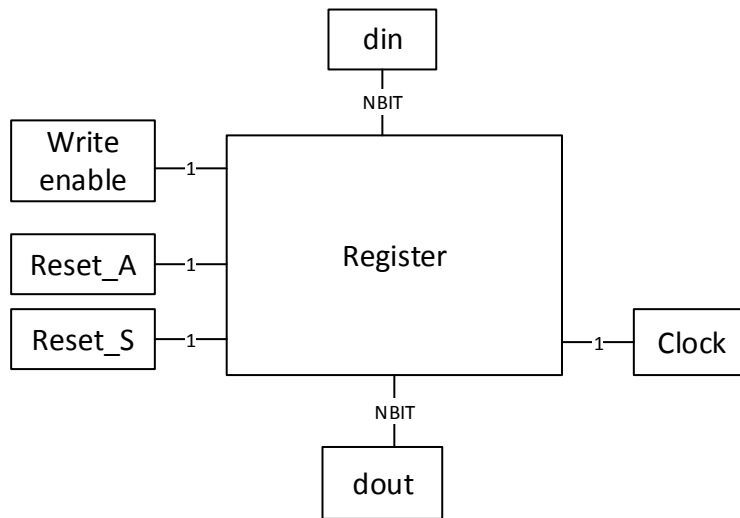


## 4 Compilation

### Register

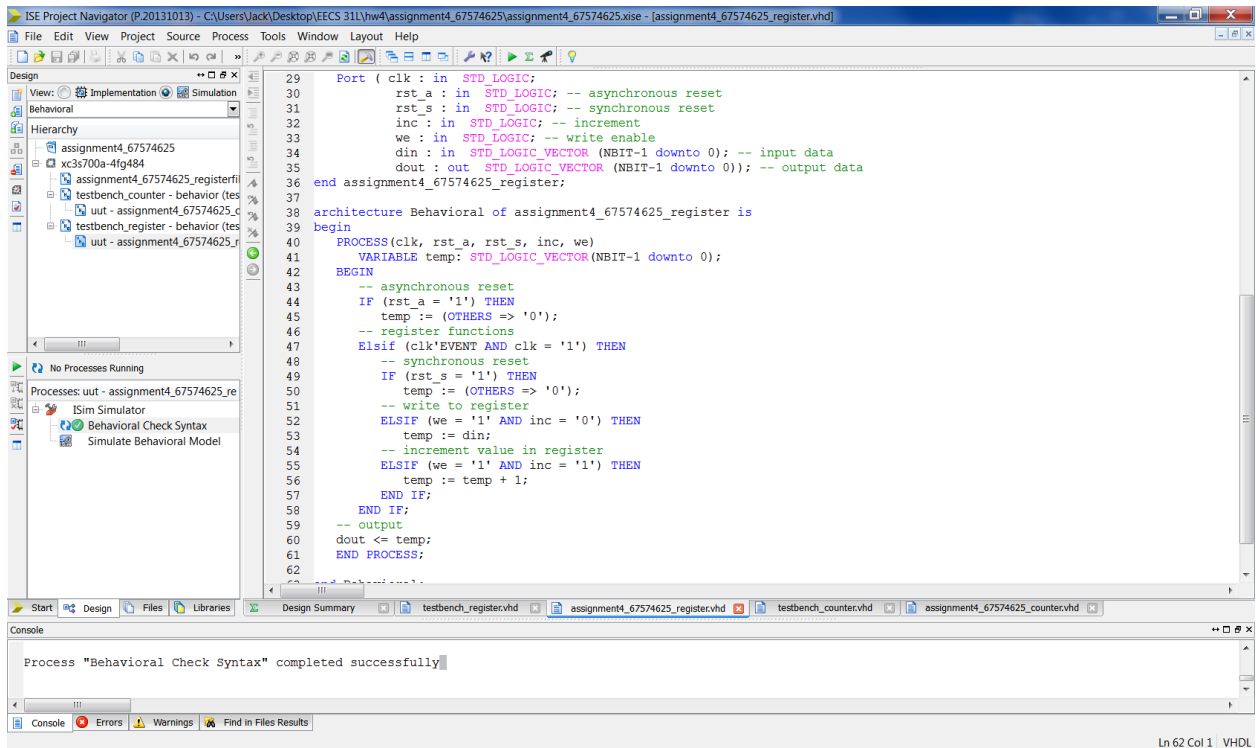

### Testbench

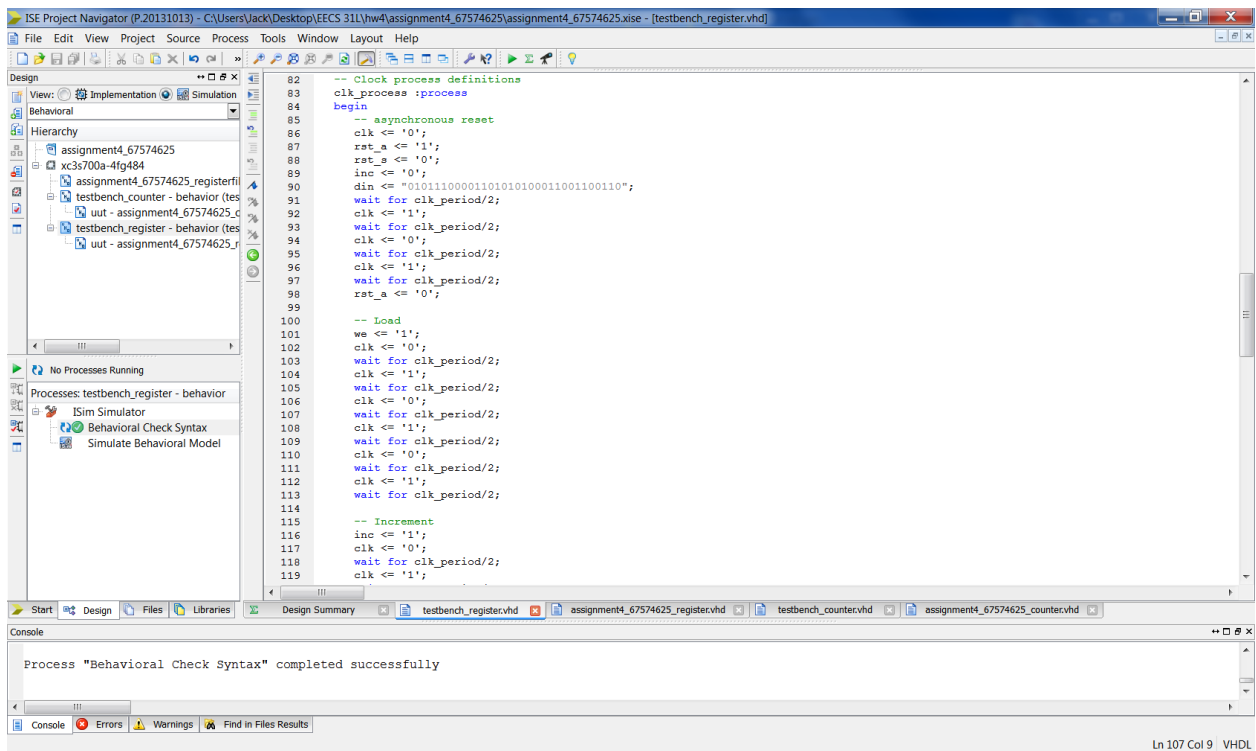

## 5 Elaboration

### Assumptions:

- Register can store any NBIT value

Regarding how I wrote my vhdl code

- I used a process with a variable called temp
- Used sequential if and elsif statements

### Errors and Challenges:

- I was having issues early on with the process statement. I didn't realize "else if" id "elsif" in VHDL
- Misusing assignment operators; tried using signal assignment operator on a variable

### Simulation Log:

Started : "Simulate Behavioral Model".

Determining files marked for global include in the design...

Running fuse...

Command Line: fuse -intstyle ise -incremental -o {C:/Users/Jack/Desktop/EECS 31L/hw4/assignment4\_67574625/testbench\_register\_isim\_beh.exe} -prj {C:/Users/Jack/Desktop/EECS 31L/hw4/assignment4\_67574625/testbench\_register\_beh.prj} work.testbench\_register { }

Running: C:\Xilinx\14.7\ISE\_DS\ISE\bin\nt64\unwrapped\fuse.exe -intstyle ise -incremental -o C:/Users/Jack/Desktop/EECS 31L/hw4/assignment4\_67574625/testbench\_register\_isim\_beh.exe -prj C:/Users/Jack/Desktop/EECS 31L/hw4/assignment4\_67574625/testbench\_register\_beh.prj work.testbench\_register

ISim P.20131013 (signature 0x7708f090)

Number of CPUs detected in this system: 4

Turning on mult-threading, number of parallel sub-compilation jobs: 8

Determining compilation order of HDL files

Parsing VHDL file "C:/Users/Jack/Desktop/EECS 31L/hw4/assignment4\_67574625/assignment4\_67574625\_register.vhd" into library work

Parsing VHDL file "C:/Users/Jack/Desktop/EECS 31L/hw4/assignment4\_67574625/testbench\_register.vhd" into library work

Starting static elaboration

Completed static elaboration

Compiling package standard

Compiling package std\_logic\_1164

Compiling package std\_logic\_arith

Compiling package std\_logic\_unsigned

Compiling package numeric\_std

Compiling architecture behavioral of entity assignment4\_67574625\_register

[assignment4\_67574625\_register(3...]

Compiling architecture behavior of entity testbench\_register

Time Resolution for simulation is 1ps.

Waiting for 1 sub-compilation(s) to finish...

Compiled 8 VHDL Units

Built simulation executable C:/Users/Jack/Desktop/EECS

31L/hw4/assignment4\_67574625/testbench\_register\_isim\_beh.exe

Fuse Memory Usage: 37152 KB

Fuse CPU Usage: 529 ms

Launching ISim simulation engine GUI...

"C:/Users/Jack/Desktop/EECS

31L/hw4/assignment4\_67574625/testbench\_register\_isim\_beh.exe" -intstyle ise -gui -tclbatch

isim.cmd -wdb "C:/Users/Jack/Desktop/EECS


31L/hw4/assignment4\_67574625/testbench\_register\_isim\_beh.wdb"

ISim simulation engine GUI launched successfully

Process "Simulate Behavioral Model" completed successfully


## 6 Waveforms

### Full Waveform Snapshot

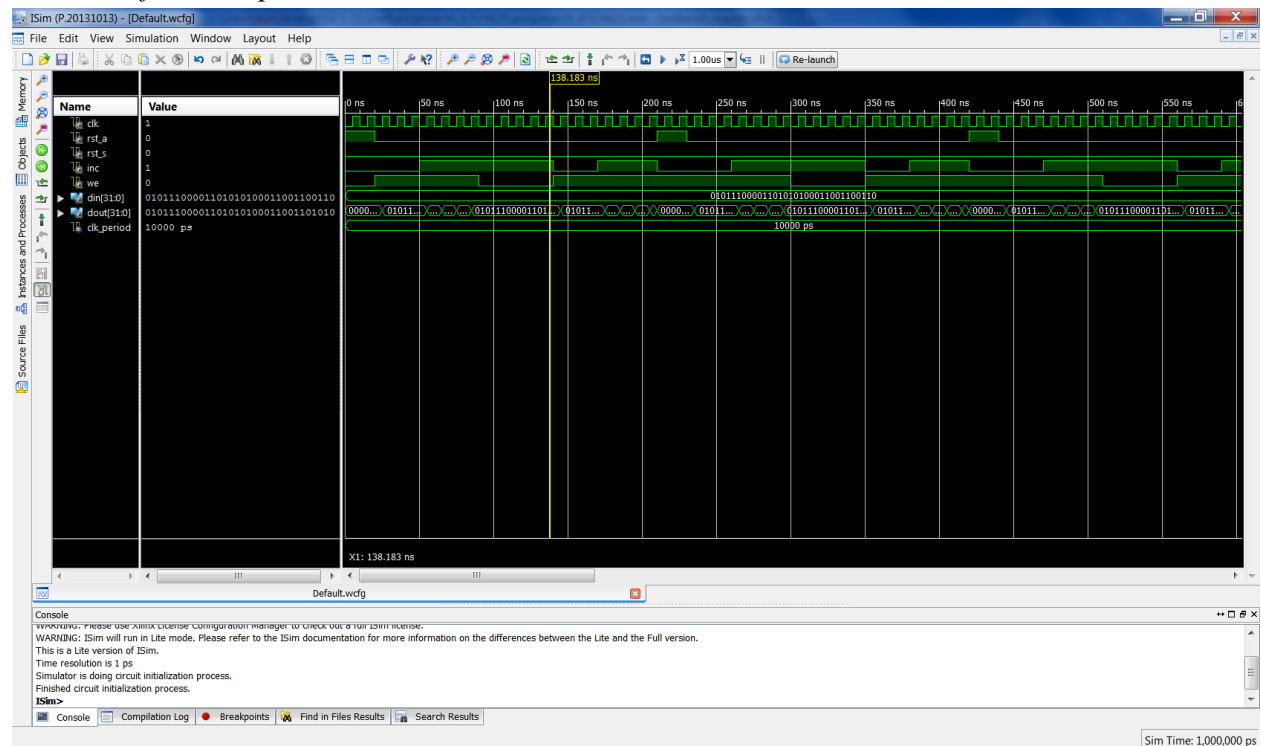


## Snapshots of Waveform


### Reset (asynchronous)

 


### Reset (synchronous)

 

### Load input

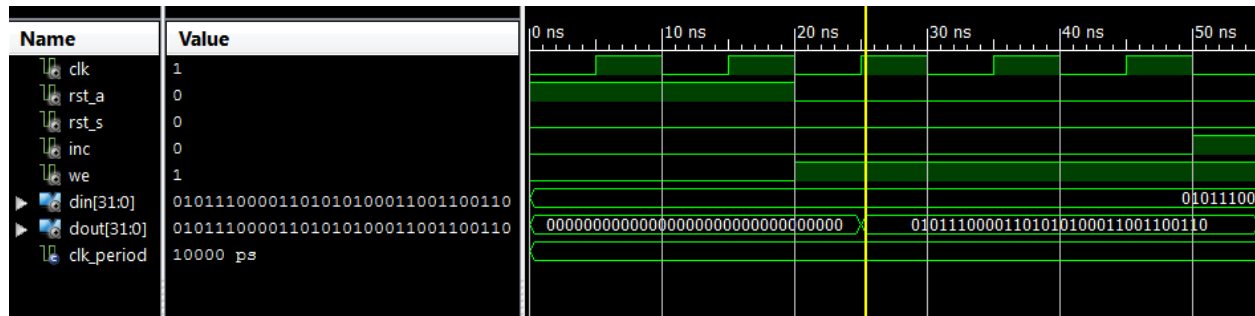

### Increment

 

### Hold (write enable off)

