

Introduction to Digital Logic

EECS/CSE 31L

Assignment 4: Counter

Prepared by: Jack Melcher

Student ID: 67574625

EECS Department
Henry Samueli School of Engineering
University of California, Irvine

February 15, 2015

1 Block Description

- Construct a counter that can be parameterized
- Can either increment or decrement
- Load the counter with a desired value
- Has a synchronous reset

2 Input/Output Port Description

Generic Name	Data Type	Default Value	Description
NBIT	INTEGER	32	Size of counter
STEP	INTEGER	1	How much the counter increments/decrements

Port name	Port size	Port Type	Description
Clk	1	IN	Triggers the counting
Rst_s	1	IN	Will reset the counter to zero when active
asc	1	IN	Increments when '1' and decrements when '0'
preload	1	IN	Trigger the counter to load a given value
din	NBIT-1 downto 0	IN	The input value
dout	NBIT-1 downto 0	OUT	The counter's value after counting


Variable Name	Data Type	Port size	Description
count	INTEGER	NBIT-1 downto 0	Aids in the counting process

3 Design Schematics

Truth Table:

Clk (Rising edge)	Rst_s	asc	preload	Function
1	1	X	X	Reset counter to zero
1	0	1	0	increment
1	0	0	0	decrement
1	0	X	1	Load din into counter

Design:

 


4 Compilation

Counter

```
architecture Behavioral of assignment4_67574625_counter is
begin
    PROCESS(clk, rst_s, asc, preload)
        VARIABLE count: STD_LOGIC_VECTOR(NBIT-1 downto 0);
    BEGIN
        -- counting functions
        IF(clk'event AND clk = '1') THEN
            -- reset counter
            IF (rst_s = '1') THEN
                count := (OTHERS => '0');
            -- load din into counter
            ELSIF(preload = '1') THEN
                count := din;
            -- increment
            ELSIF(preload = '0' AND asc = '1') THEN
                count := count + STEP;
            -- When most significant bit becomes '1'
            IF(count(NBIT-1) = '1') THEN
                count := (OTHERS => '0');
            END IF;
            -- decrement
            ELSIF(preload = '0' AND asc = '0') THEN
                count := count - STEP;
            -- When most significant bit becomes '1'
            IF(count(NBIT-1) = '1') THEN
                count := (NBIT-1=>'0',OTHERS => '1');
            END IF;
            END IF;
        -- output
        dout <= count;
    END PROCESS;
```

Process "Behavioral Check Syntax" completed successfully

Testbench

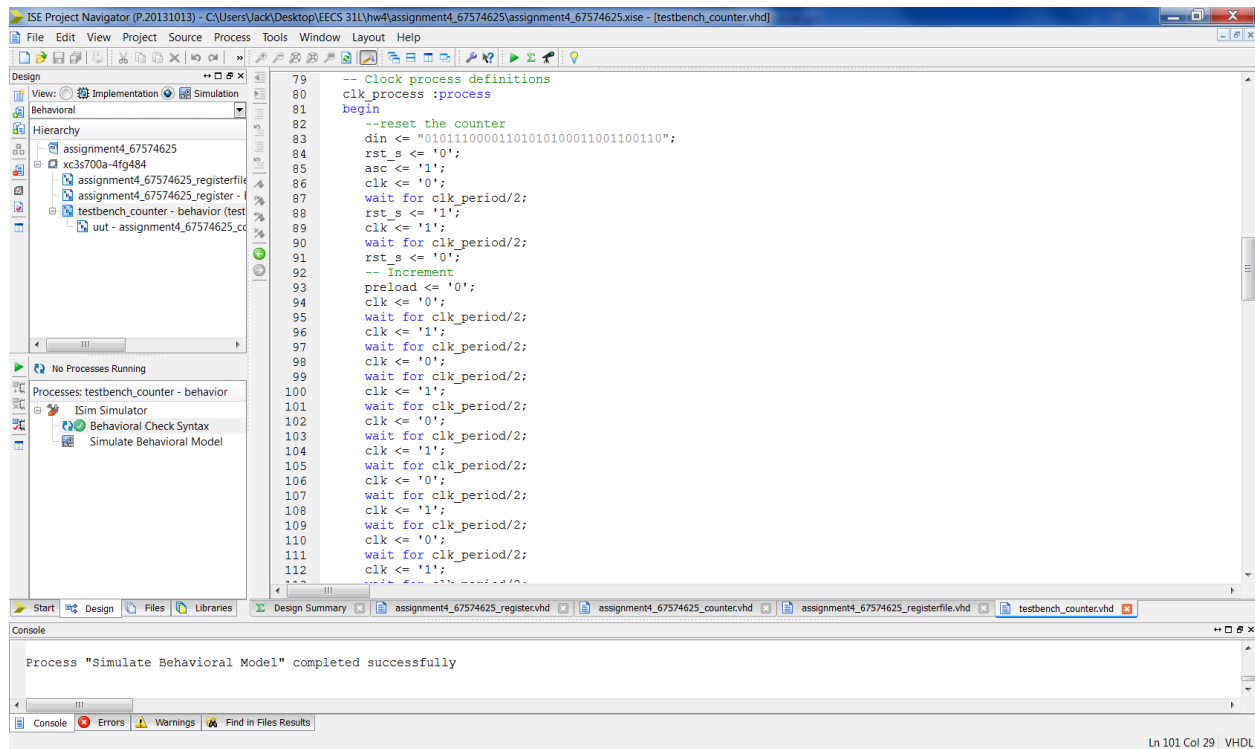

5 Elaboration

Assumptions:

- The counter cannot output a negative value
- The most significant bit will result in the negative value
 - Counter loops back to zero if incrementing
 - Counter loops back to the greatest positive value it can take

Regarding how I wrote my vhd code

- I used a process with a variable called count
- Used sequential if and elsif statements

Errors and Challenges:

- I was having issues early on with the process statement. I didn't realize "else if" id "elsif" in VHDL
- Misusing assignment operators; tried using signal assignment operator on a variable

Simulation Log:

Started : "Simulate Behavioral Model".

Determining files marked for global include in the design...

Running fuse...

Command Line: fuse -intstyle ise -incremental -o {C:/Users/Jack/Desktop/EECS
31L/hw4/assignment4_67574625/testbench_counter_isim_beh.exe} -prj
{C:/Users/Jack/Desktop/EECS 31L/hw4/assignment4_67574625/testbench_counter_beh.prj}
work.testbench_counter { }

Running: C:\Xilinx\14.7\ISE_DS\ISE\bin\nt64\unwrapped\fuse.exe -intstyle ise -incremental -o
C:/Users/Jack/Desktop/EECS 31L/hw4/assignment4_67574625/testbench_counter_isim_beh.exe
-prj C:/Users/Jack/Desktop/EECS 31L/hw4/assignment4_67574625/testbench_counter_beh.prj
work.testbench_counter

ISim P.20131013 (signature 0x7708f090)

Number of CPUs detected in this system: 4

Turning on mult-threading, number of parallel sub-compilation jobs: 8

Determining compilation order of HDL files

Parsing VHDL file "C:/Users/Jack/Desktop/EECS
31L/hw4/assignment4_67574625/assignment4_67574625_counter.vhd" into library work

Parsing VHDL file "C:/Users/Jack/Desktop/EECS
31L/hw4/assignment4_67574625/testbench_counter.vhd" into library work

Starting static elaboration

Completed static elaboration

Compiling package standard

Compiling package std_logic_1164

Compiling package std_logic_arith

Compiling package std_logic_unsigned

Compiling package numeric_std

Compiling architecture behavioral of entity assignment4_67574625_counter
[assignment4_67574625_counter(32...)]

Compiling architecture behavior of entity testbench_counter

Time Resolution for simulation is 1ps.

Compiled 8 VHDL Units

Built simulation executable C:/Users/Jack/Desktop/EECS
31L/hw4/assignment4_67574625/testbench_counter_isim_beh.exe

Fuse Memory Usage: 37152 KB

Fuse CPU Usage: 561 ms

Launching ISim simulation engine GUI...


"C:/Users/Jack/Desktop/EECS
31L/hw4/assignment4_67574625/testbench_counter_isim_beh.exe" -intstyle ise -gui -tclbatch

isim.cmd -wdb "C:/Users/Jack/Desktop/EECS
31L/hw4/assignment4_67574625/testbench_counter_isim_beh.wdb"
ISim simulation engine GUI launched successfully

Process "Simulate Behavioral Model" completed successfully


6 Waveforms

Full Waveform Snapshot

 


Snapshots of Waveform


Reset Counter

 


Increment

 


Decrement

 


Load random value and start Incrementing

 

 Load greatest positive value and loop back to zero and continue incrementing



Load random value and start Decrementing

 

Load zero and loop back to greatest positive value and continue decrementing

